

Motor driver

DO

OUTPUT

MOVEMENT


What does it do?

A motor driver lets a low-power GPIO control a motor that needs more current.

The L293D contains H-bridges that can send current through a motor in either direction.

Two input pins choose forwards, backwards or stop, while the chip handles the motor current.

Uses

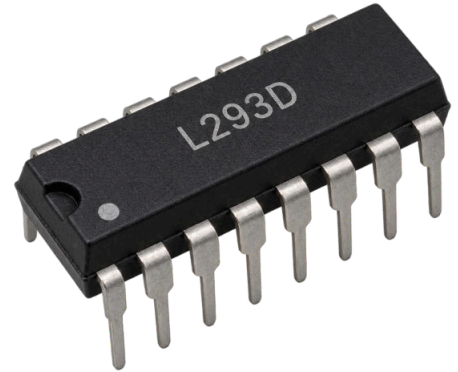

Electric car window

DETECT

Read window switch




DECIDE

Choose up or down



DO

Drive the window motor

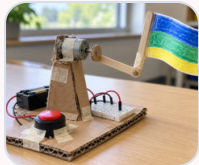

Tiny flag waver

DETECT

Victory button pressed



DECIDE

Is celebration required



DO

Wave the flag

Notch
Identifies pin 1

IN1 and IN2
Direction controls

OUT1 and OUT2
Connect to the motor

Enable
Held high in this circuit

Code

● Raspberry Pi

```
from gpiozero import Motor
motor = Motor(forward=17, backward=18)
motor.forward()
```


● Raspberry Pi Pico

```
from picozero import Motor
motor = Motor(14, 15)
motor.forward()
```

This card powers one small 5 V motor from the board's 5 V rail. Use a separate motor supply for larger motors, with the grounds joined.


Wiring

RASPBERRY PI 5

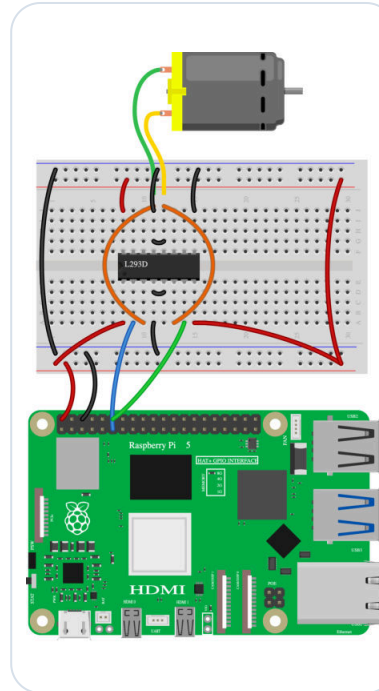

GPIO17 → IN1, **GPIO18** → IN2; OUT1 and OUT2 → motor

PICO

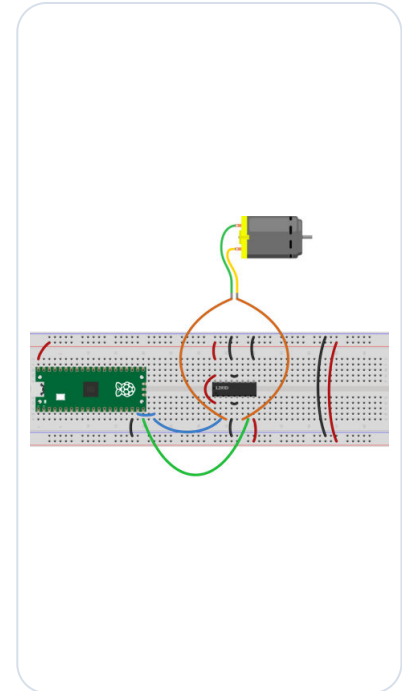

GP14 → IN1, **GP15** → IN2; OUT1 and OUT2 → motor