Motor driver

DO | PICO BLOCKS | OUTPUT | MOVEMENT

What does it do?

A motor driver lets a low-power GPIO control a motor that needs more current.

The L293D contains H-bridges that can send current through a motor in either direction.


Two input pins choose forwards, backwards or stop, while the chip handles the motor current.

Uses




Electric car window

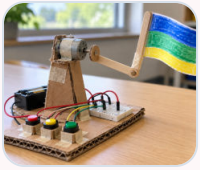DETECT Read window switch → **DECIDE** Can it move safely? → **DO** Drive requested direction



Tiny flag waver

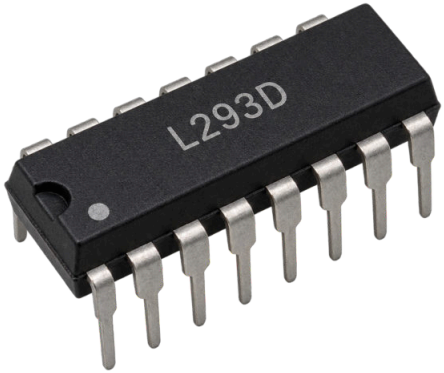DETECT Count score-button presses → **DECIDE** Has the target been reached? → **DO** Wave the flag



Notch
Identifies pin 1

IN1 and IN2
Direction controls


OUT1 and OUT2
Connect to the motor

Enable
Held high in this circuit

Blocks

MicroLab


getmicrolab.com

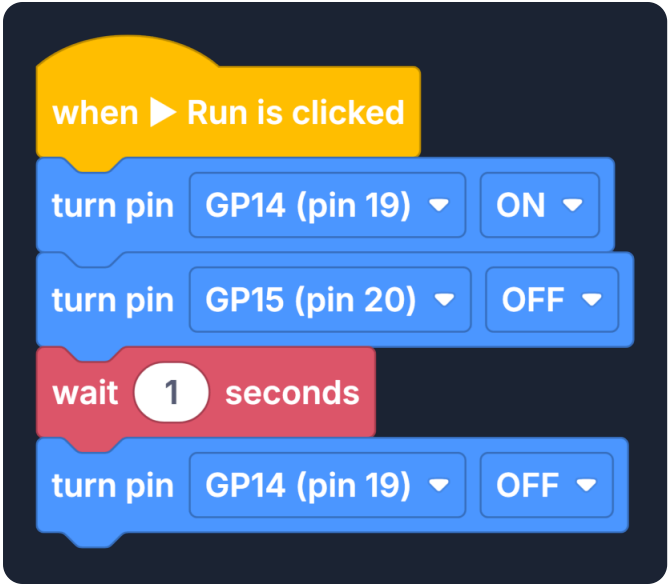

GP14 ON and GP15 OFF drive forwards for one second. Swap them to go backwards.

Wiring

PICO

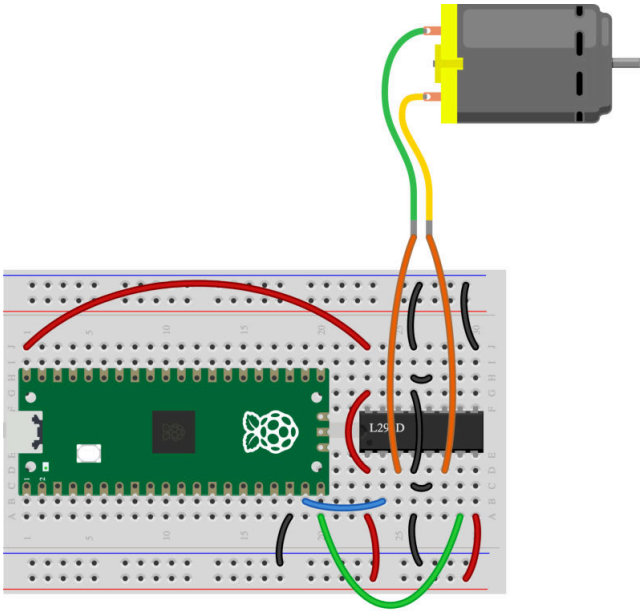

GP14 (pin 19) → IN1, **GP15** (pin 20) → IN2; OUT1 and OUT2 → motor; **VBUS** (pin 40), **GND** (pin 18)