Motor driver

DO | RASPBERRY PI | OUTPUT | MOVEMENT

What does it do?

A motor driver lets a low-power GPIO control a motor that needs more current.

The L293D contains H-bridges that can send current through a motor in either direction.


Two input pins choose forwards, backwards or stop, while the chip handles the motor current.

Uses




Electric car window

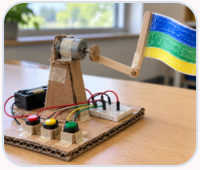DETECT Read window switch → **DECIDE** Can it move safely? → **DO** Drive requested direction



Tiny flag waver

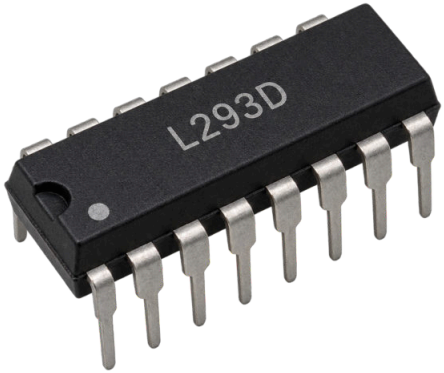DETECT Count score-button presses → **DECIDE** Has the target been reached? → **DO** Wave the flag



Notch
Identifies pin 1

IN1 and IN2
Direction controls

OUT1 and OUT2
Connect to the motor

Enable
Held high in this circuit

Code

Raspberry Pi

```
from gpiozero import Motor


motor = Motor(forward=17, backward=27)

motor.forward()
```

This card powers one small 5 V motor from the board's 5 V rail. Use a separate motor supply for larger motors, with the grounds joined.

Wiring

RASPBERRY PI 5

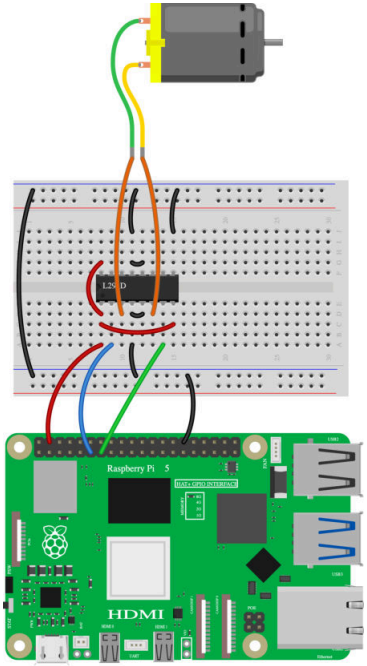

GPIO17 (pin 11) → IN1, **GPIO27** (pin 13) → IN2; OUT1 and OUT2 → motor; **5V** (pin 4), **GND** (pin 30)