Motor driver

DO | PICO | OUTPUT | MOVEMENT

What does it do?

A motor driver lets a low-power GPIO control a motor that needs more current.

The L293D contains H-bridges that can send current through a motor in either direction.


Two input pins choose forwards, backwards or stop, while the chip handles the motor current.

Uses




Electric car window

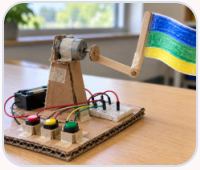DETECT Read window switch → **DECIDE** Can it move safely? → **DO** Drive requested direction



Tiny flag waver

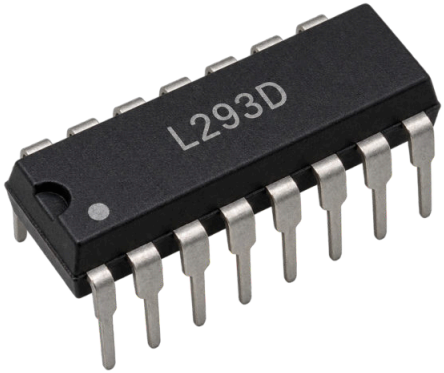DETECT Count score-button presses → **DECIDE** Has the target been reached? → **DO** Wave the flag



Notch
Identifies pin 1

IN1 and IN2
Direction controls

OUT1 and OUT2
Connect to the motor

Enable
Held high in this circuit

Raspberry Pi Foundation

Code

Raspberry Pi Pico

```
from picozero import Motor


motor = Motor(14, 15)

motor.forward()
```

This card powers one small 5 V motor from the board's 5 V rail. Use a separate motor supply for larger motors, with the grounds joined.

Wiring

PICO

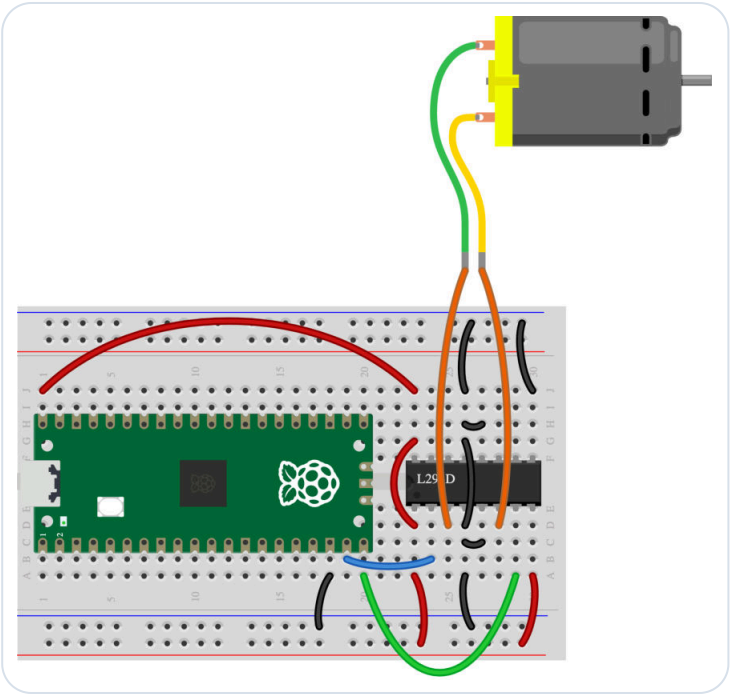

GP14 (pin 19) → IN1, **GP15** (pin 20) → IN2; OUT1 and OUT2 → motor; **VBUS** (pin 40), **GND** (pin 18)