Toggle switch

DETECT | RASPBERRY PI | INPUT

What does it do?

A toggle switch stays in the position you move it to, unlike a push button.

Its centre COM leg connects to one outside leg in each position.


It is useful when a project needs a lasting on/off choice or two modes.

Uses



Auto/manual selector

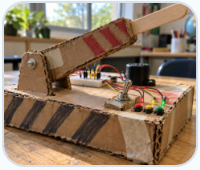DETECT Read selector position → **DECIDE** Is automatic mode selected? → **DO** Run the selected mode



Serious business lever

DETECT Lever and check buttons → **DECIDE** Are all checks complete? → **DO** Start unnecessary sirens



Lever	COM	L1 and L2
Stays where it is moved	Centre pin	The two choices

Code

Raspberry Pi

```
from gpiozero import Button


mode = Button(3)

mode_two = mode.is_pressed
```

Connect COM and one outside pin. The unused outside pin can be left unconnected.

Wiring

RASPBERRY PI 5

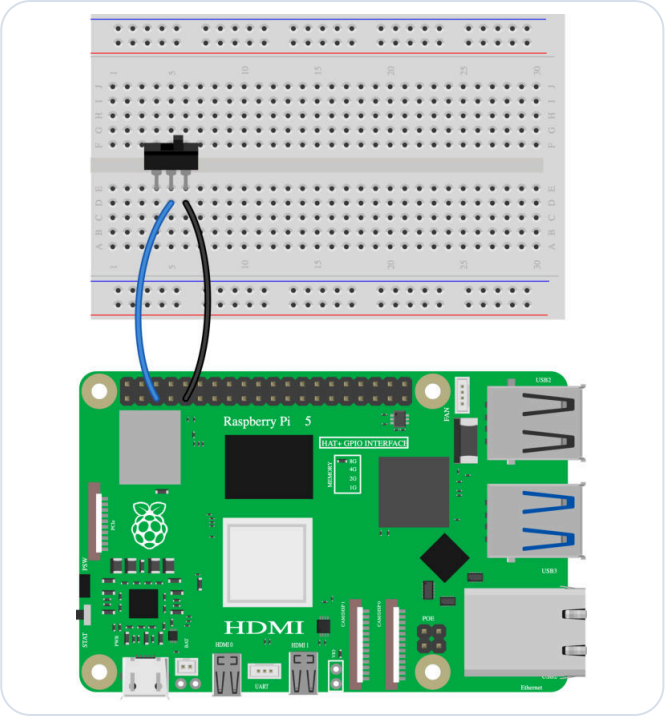

GPIO 3 (pin 5) → COM; right-hand outside pin → **GND** (pin 9)